

Logic Design

Lecture 2

September 17, 2019

Logic

All switches in a logic circuit have to be closed to get an output of 1.

Symbols

- OR- +
- AND- .
- NOT- !

Functions

- To get the number of states of a circuit with n switches, get 2^n When serializing circuits that have